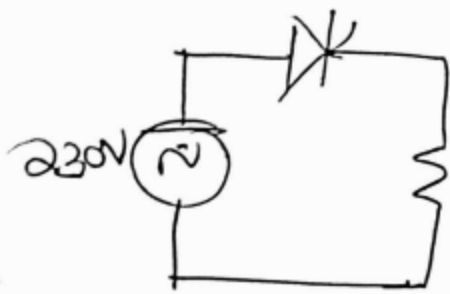


## Power Electronics

2. Thyristor is connected in series with  $100\Omega$  resistor to a  $230V$  sinusoidal supply. If the thyristor is controlled to switch on at a firing angle of  $30^\circ$ , determine the average current in the thyristor.



Given :

$$\alpha = 30^\circ$$

$$V_{rms} = 230V$$

$$R = 100\Omega$$

$$I_0 = ?$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_m = V_{rms} \times \sqrt{2}$$
$$= 230 \times \sqrt{2}$$


$$V_m = 325.26V$$

$$I_0 = \frac{V_m}{R} = \frac{V_m (1 + \cos \alpha)}{R \cdot 2\pi}$$

$$= \frac{325.26 (1 + \cos 30^\circ)}{100 \times 2 \times 3.142}$$

$$I_0 = 0.96558 A$$

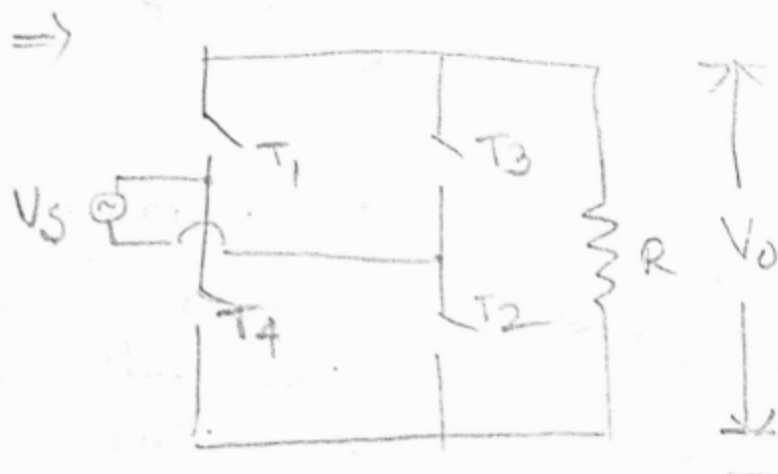2. A SCR Fully controlled bridge rectifier is connected in series with a  $200\Omega$  resistor to a  $230V$  sinusoidal supply. If the SCR is controlled to switch on at a firing angle of  $60^\circ$ , determine the average output current.



$$\begin{aligned}
 R &= 200\Omega \\
 V_{rms} &= 230V \\
 \alpha &= 60^\circ \quad \left| \quad V_m = V_{rms} \times \sqrt{2} \right. \\
 I_o &= ? \quad \left| \quad \begin{aligned} &= 230 \times \sqrt{2} \\ &V_m = 325.26V \end{aligned} \right.
 \end{aligned}$$

$$I_o = \frac{V_o}{R} = \frac{V_m}{\pi \times R} (1 + \cos \alpha) = \frac{325.26 (1 + \cos 60^\circ)}{\pi \times 200}$$

$$\boxed{I_o = 0.776A}$$