

# Problems:

## Of Power Electronics & Batteries

**Problem 1:** A thyristor is connected in series with a **100  $\Omega$**  resistor to a **230 V (rms) sinusoidal supply**. If the thyristor is controlled to switch on at a **firing angle of  $30^\circ$** , determine the average current in the thyristor.

Solution :

The described circuit is half wave controlled rectifier

Given data:  $R = 100 \Omega$ ,  $V_{\text{rms}} = 230 \text{ V}$ , Firing angle =  $30^\circ$ .

Governing equations:

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$I_o = \frac{V_o}{R} = \frac{V_m}{R} \cdot \frac{1}{2\pi} (1 + \cos \alpha)$$

**Problem 2:** A sinusoidal source of  $v = 325.26 \sin(\omega t)$  is applied as input to the full-bridge controlled rectifier feeding resistor of  $15 \Omega$ . The average output current measured flowing through the resistance is  $12.5 \text{ A}$ . Calculate the operating firing angle of the circuit and the average output voltage.

Solution: The circuit is bridge controlled rectifier

Given data:  $v = 325.26 \sin(\omega t)$ ,  $R = 15 \Omega$ ,  $I_0 = 12.5 \text{ A}$

To find: the operating firing angle and  $V_0$ .

Governing equations:

$$I_o = \frac{V_o}{R} = \frac{V_m}{R} \cdot \frac{1}{\pi} (1 + \cos \alpha) \quad \text{Find alpha using this equation}$$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

**Problem 3:** Assume that 20 Dry cells of 1.45 V emf are connected in series. When an external resistance of 12 Ohms is connected in series with the battery, the value of current flow is 2A. What is the value of internal resistance of each cell?

$$I = \frac{nE}{R + nr} \text{ Amperes}$$

$$r = \frac{nE}{nI} - \frac{R}{n} \text{ Amperes}$$

Ans.: 0.125 Ohms

**Problem 4:** A battery is formed of six cells connected in series. When the external resistance of 3 Ohms is joined across its terminals, the current is found to be 2.5 A and when it is 9 Ohms the current falls to 1.25 A. Find the emf of each cell and its internal resistance.

$$I = \frac{nE}{R + nr} \text{ Amperes}$$

First case

$$7.5 + 15r = 6E$$

$$\text{Ans.: } r = 0.50\text{Ohms}$$

Second Case

$$11.25 + 7r = 6E$$

$$E = 2.5 \text{ Volts}$$

**Problem 5:** Calculate the i.) Ampere hour efficiency and ii.) Watt-hour efficiency of a secondary cell which is discharged at a uniform rate of 30 A for 6 hours at an average terminal voltage of 2 V. It is then charged at the uniform rate of 40 A for 5 hours to restore it to its original condition. The terminal voltage during charging is 2.5 V

Solution:

**First case**

$$\text{A h output} = 30 \times 6 =$$

$$\text{A h Input} = 40 \times 5 =$$

**Ans.: A h- efficiency % = 90%**

**Second Case**

The terminal voltage during charging is 2.5 V

$$\text{W -h output} = 2 \times 30 \times 6 =$$

$$\text{W- h input} = 2.5 \times 40 \times 5 =$$

**Ans.: W h- efficiency % = 72%**

$$\text{A h efficiency}(\eta_{Ah}) \% = \frac{\text{Amperehours on discharging}}{\text{Amperehours on charging}} \times 100$$

# Thank You