



**KLE** Technological  
University

Creating Value  
Leveraging Knowledge

## **Unit –I**

### Chapter 3

# Transistor

# Contents

Session No.	Contents covered
01	BJT, transistor voltages and currents, Signal amplifier (Fixed bias, Collector base bias, Voltage divider bias, CE configuration)
02	DC load line (Q-point), Voltage, current and power gains
03	Transistor as a switch: NOT Gate, Basic (DTL) NAND gate.

# Topic Learning Outcomes

*At the end of the topic, students should be able to:*

- 1.Discuss on the transistor CE configuration.
- 2.Explain significance of DC load line and operating point.
- 3.Realize the simple applications using transistor.


**CO-2: Describe the characteristics of semiconductor devices and their applications in rectifiers, switches, regulators and gates.**

# Key concepts

1. Transistor construction and operation
2. Transistor voltages and currents
3. Common emitter input and output characteristics
4. DC Load line & Q Point
5. Transistor biasing
6. Base bias circuit
7. Collector base circuit
8. Voltage divider circuit
9. Transistor as switch: NOT gate and DTL NAND gate

 
# Transistor Definition

- Transistor is an electronic device made of three layers of semiconductor material that can act as insulator and a conductor.
- The three layered transistor is also known as the bipolar junction transistor.


 
# Bipolar Junction Transistors(BJT's)

- It can be used as amplifier and logic switches.
- BJT consists of three terminals:
  - Collector: C
  - Base: B
  - Emitter: E
- Two types of BJT : npn and pnp




# Transistor Construction

- 3 layer semiconductor device consists of :
  - 2 n- and 1 p- type layers of material ->npn transistor
  - 2 p- and 1 n- type layers of material ->pnp transistor
- A single pn junction has two different types of bias:
  - Forward bias
  - Reverse bias
- Thus, a two-pn-junction device has four types of bias.
 
# Position of terminals and symbol of BJT


- **Base** is located at the middle and more thin from the level of collector and emitter.
- The **collector** and **emitter** terminals are made of the same type of semiconductor material, while the base of the other type material.





# Transistor currents

 1. The arrow is always drawn on the emitter
2. The arrow always points toward the n-type.
3. The arrow indicates the direction of emitter current:



pnp: E→B

npn: B→E


$I_C$  = Collector current

$I_B$  = Base current


$I_E$  = Emitter current

# Transistor Voltages

 1. The supply voltage between the base and the emitter is denoted by  $V_{BE}$ .
2. The supply voltage between the collector and the base is denoted by  $V_{CB}$ .
3. The collector is biased to a higher negative level than the base to keep the collector-base junction reverse biased.



# NPN Transistor operation

 


Working of NPN Transistor

1. The base-emitter junction is connected in the forward bias condition by supply voltage  $V_{EE}$ .
2. And the collector-base junction is connected in the reverse bias condition by supply voltage  $V_{CC}$ .
3. The depletion region of the emitter-base region is thin compared to the depletion region of the collector-base junction

# NPN Transistor operation

4. In N-type emitter, the majority charge carrier is electrons. the current will start flowing the emitter-base junction. This current is known as emitter current  $I_E$ .
5. These electrons move further to the base. The base is a P-type semiconductor. Therefore, it has holes. But the base region is very thin and lightly doped.
6. So, it has a few holes to recombine with the electrons. Hence, most of the electrons will pass the base region and few of them will recombine with the holes.
7. Because of the recombination, the current will flow through the circuit and this current is known as base current  $I_B$ .

# PNP Transistor operation

 

Working of PNP Transistor

1. The positive terminal of a voltage source ( $V_{EB}$ ) is connected with Emitter (P-type) and the negative terminal is connected with the Base terminal (N-type). Therefore, the Emitter-Base junction is connected in forward bias.
2. And the positive terminal of a voltage source ( $V_{CB}$ ) is connected with the Base terminal (N-type) and the negative terminal is connected with the Collector terminal (P-type). Hence, the Collector-Base junction is connected in reverse bias.

# PNP Transistor operation

4. The depletion region at Emitter-Base junction is narrow, because it is connected in forward bias. While the Collector-Base junction is in reverse bias and hence the depletion region at Collector-Base junction is wide.

5. The Emitter-base junction is in forward bias. Therefore, a very large number of holes from emitter cross the depletion region and enter the Base. Simultaneously, very few electrons enter in Emitter from the base and recombine with the holes.

6. Because of the movement of holes, the current will flow through the Emitter-Base junction. This current is known as Emitter current ( $I_E$ ). The holes are majority charge carriers to flow the Emitter current.

7. The remaining holes which do not recombine with electrons in Base, that holes will further travel to the Collector. The Collector current ( $I_C$ ) flows through the Collector-Base region due to holes.

# $\alpha_{dc}$ and $\beta_{dc}$ for a transistor

$\alpha_{dc}$  is emitter to collector current gain. It is the ratio of collector to emitter current i.e.,

$$\alpha_{dc} = \frac{I_C}{I_E}$$

Where  $I_C$  is dc collector current and  $I_E$  is dc emitter current.

$\beta_{dc}$  is base to collector current gain. It is the ratio of collector to base current i.e.,


$$\beta_{dc} = \frac{I_C}{I_B}$$

Where  $I_B$  is dc Base current.

$\beta_{dc}$  is commonly known as  $h_{FE}$  based on h-parameter analysis of transistor.

$$h_{FE} = \frac{I_C}{I_B}$$

# Equation for collector current

 

From figure

$$I_E = I_C + I_B \quad \dots\dots\dots 1$$

By definition

$$\alpha_{dc} = \frac{I_C}{I_E} \quad \dots\dots\dots 2$$

$$\text{or } I_C = \alpha_{dc} I_E \quad \dots\dots\dots 3$$

From equations 1 & 3

$$I_C = \alpha_{dc}(I_C + I_B)$$

Or

$$I_C = \alpha_{dc} I_C + \alpha_{dc} I_B$$

$$I_C = \frac{\alpha_{dc}}{1 - \alpha_{dc}} I_B$$



# Relationship between $\alpha_{dc}$ and $\beta_{dc}$

$$\beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}}$$


$\beta_{dc}$  in terms of  $\alpha_{dc}$

$$\alpha_{dc} = \frac{\beta_{dc}}{1 + \beta_{dc}}$$
 
# Problem 1

For the circuit shown below find:


- Values of  $\alpha_{dc}$  and  $\beta_{dc}$  of the transistor
- Value of  $I_B$  for a desired  $I_C$  of 5mA



## Problem 2


Find the values of  $I_C$  and  $I_E$  for a transistor with  $\alpha_{dc}=0.97$  and  $I_B=50\mu A$ . Find  $\beta_{dc}$  of transistor used.

# Common-emitter input characteristics

 


1. The base to emitter voltage varies by adjusting the potentiometer  $R_1$ . And the collector to emitter voltage varied by adjusting the potentiometer  $R_2$ .
2. For the various setting, the current and voltage are taken from the milliammeters and voltmeter. On the basis of these readings, the input and output curve plotted on the curve

# Common-emitter input characteristics

 

1. The curve plotted between base current  $I_B$  and the base-emitter voltage  $V_{BE}$  is called Input characteristics curve.
2. For drawing the input characteristic the reading of base currents is taken through the ammeter on emitter voltage  $V_{BE}$  at constant collector-emitter current.
3. The base current  $I_B$  increases with the increases in the emitter-base voltage  $V_{BE}$ .

# Common-emitter output characteristics

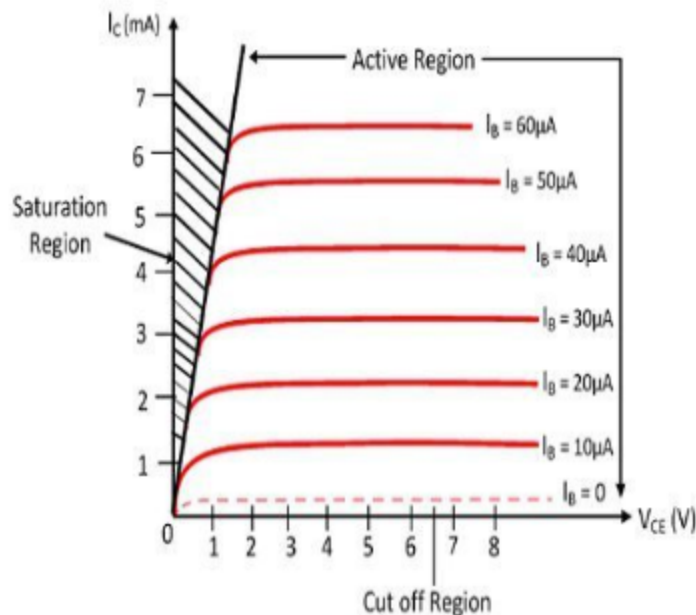


1. The curve draws between collector current  $I_C$  and collector-emitter voltage  $V_{CE}$  at a constant base current  $I_B$  is called output characteristic.
2. In the active region, the collector current increases slightly as collector-emitter  $V_{CE}$  current increases. The slope of the curve is quite more than the output characteristic of CB configuration.
3. When the  $V_{CE}$  falls, the  $I_C$  also decreases rapidly. The collector-base junction of the transistor always in forward bias and work saturate.

# DC Load line

1. DC Load line for a transistor circuit is a straight line drawn on transistor output characteristics.
2. For a common emitter( $C_E$ ) circuit, the load line is a graph of collector current( $I_C$ ) versus collector-emitter voltage ( $V_{CE}$ ), for a given value of collector resistance( $R_C$ ) and a given supply voltage( $V_{CC}$ ).

# Procedure for drawing DC Load line

 

The dc supply voltage  $V_{CC}$  forward biases base-emitter and reverse biases collector-base junction.

Apply KVL to base-emitter circuit

$$V_{CC} = I_B R_B + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$



# Procedure for drawing DC Load line

The collector current is given by,

$$I_C = h_{FE} I_B$$

Apply KVL to collector-emitter circuit

$$V_{CC} = I_C R_C + V_{CE}$$

**To obtain A**

When  $V_{CE} = 0$ , the  $I_C$  is maximum and is equal to  $V_{CC}/R_C$ .


This gives the maximum value of  $V_{CE}$ . This is shown as:

$$V_{CE} = V_{CC} - I_C R_C \quad V_{CE} = V_{CC} - I_C R_C$$

$$0 = V_{CC} - I_C R_C \quad 0 = V_{CC} - I_C R_C$$

$$I_C = \frac{V_{CC}}{R_C} \quad I_C = \frac{V_{CC}}{R_C}$$

 This gives the point A ( $OA = V_{CC}/R_C$ ) on  $I_C$  axis, shown in the figure.



# Procedure for drawing DC Load line

## To obtain B


When the  $I_C = 0$ , then  $V_{CE}$  is maximum and will be equal to the  $V_{CC}$ .

This gives the maximum value of  $I_C$ .


This is shown as

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C \\ V_{CE} &= V_{CC} - I_C R_C \\ &= V_{CC} = V_{CC} \\ (\text{As } I_C &= 0) \end{aligned}$$

 This gives the point B, which means ( $OB = V_{CC}$ ) on The collector voltage axis shown in the above figure.



# Q-Point

 

1. The dc bias point or Q point also known as dc operating point.
2. It identifies the transistor collector current and collector-emitter voltage when there is no input signal at base terminal.
3. The intersection of dc load line with output characteristics curve gives the coordinates of the Q point

# Transistor biasing


1. Transistor needs to be operated in an appropriate region based on the application of circuit.
2. When transistor is used as amplifier it must be in active region i.e., base-emitter is forward biased and collector-base junction is reverse biased.
3. The dc voltages and currents in circuit are established by using resistance network .
4. This process is called biasing and resistance network is called bias circuit.

# Transistor biasing

## Three biasing circuits

1. Base bias circuit
2. Collector-base bias circuit
3. Voltage divider bias circuit

# Base bias circuit

 

Apply KVL to base emitter circuit

$$V_{CC} = I_B R_B + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \quad \dots\dots\dots 1$$

As  $V_{BE} = 0.7V$  for SI and  $0.3V$  for GE  $V_{CC} \gg V_{BE}$

Therefore eqn 1 will be


$$I_B = \frac{V_{CC}}{R_B} \quad I_C = h_{FE} I_B$$

Apply KVL to collector emitter circuit

$$V_{CC} = I_C R_C + V_{CE}$$

$$V_{CE} = V_{CC} - I_C R_C$$
 
# Procedure for design of Base bias circuit



The values of  $V_{CC}$ ,  $V_{CE}$ ,  $V_{BE}$ ,  $I_C$  and  $h_{FE}$  will be given.  
The design steps are as follows

1. Calculate  $R_C$  using the relation

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} \dots\dots\dots 1$$

2. Then calculate  $I_B$  using relation


$$I_B = \frac{I_C}{h_{FE}}$$

3. Finally calculate  $R_B$  using relation

$$R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

 
## Problem 2

For the base bias circuit shown below, find  $I_B$ ,  $I_C$  and  $V_{CE}$  if  $R_C = 2.2\text{k}\Omega$ ,  $R_B = 470\text{k}\Omega$ ,  $V_{CC} = 18\text{V}$ ,  $h_{FE} = 100$ ,  $V_{BE} = 0.7\text{V}$ . Draw DC load line and indicate the Q point.





# Collector-to-base bias circuit

 

Apply KVL to path  $V_{CE}$ ,  $I_B R_B$  and  $V_{BE}$

$$V_{CE} - I_B R_B - V_{BE} = 0 \quad \dots\dots\dots 1$$

$$V_{CE} = I_B R_B + V_{BE} \quad \dots\dots\dots 2$$

$$I_B = \frac{V_{CE} - V_{BE}}{R_B}$$

Apply KVL to collector-emitter circuit,


$$V_{CC} - R_C(I_B + I_C) - V_{CE} = 0$$

$$V_{CE} = V_{CC} - R_C(I_B + I_C) \quad \dots\dots\dots 3$$

Substitute  $V_{CE}$  from eqn 1 in eqn 3,

$$I_B R_B + I_B R_C + I_C R_C = V_{CC} - V_{BE}$$

# Collector-to-base bias circuit

 

Using  $I_C = h_{FE} I_B$


$$I_B R_B + I_B R_C + h_{FE} I_B R_C = V_{CC} - V_{BE} \quad \dots\dots\dots 1$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + h_{FE}) R_C} \quad \dots\dots\dots 2$$

Stability of the operating point  
If  $I_C$  increases above design level,

- $I_C R_C$  increases
- $V_{CE}$  decreases
- $I_B$  decreases
- $I_C = h_{FE} I_B$  decreases
 
# Design procedure of Collector-to-base bias circuit



The values of  $V_{CC}$ ,  $V_{CE}$ ,  $V_{BE}$ ,  $I_C$  and  $h_{FE}$  will be given.

The design steps are as follows

1. Calculate  $I_B$  using the relation

$$I_B = \frac{I_C}{h_{FE}}$$

2. Then calculate  $R_C$  using relation


$$R_C = \frac{V_{CC} - V_{CE}}{I_C + I_B}$$

3. Then calculate  $R_B$  using relation

$$R_B = \frac{V_{CE} - V_{BE}}{I_B}$$
 
# Problem 3

For the collector-to-base bias circuit shown below, Determine the  $V_{CE}$  and  $I_C$  levels. The circuit has  $V_{CC}=15V$ ,  $R_C=1.8k\Omega$ ,  $R_B=39K\Omega$ ,  $V_{BE}=0.7V$ ,  $h_{FE}=50$ ,  $V_{BE}=0.7V$ . Draw DC load line and indicate the Q point.



# Voltage divider bias circuit (approximate analysis)

 


Fig. Voltage divider bias circuit

Also known as emitter current bias

From fig:

$$I_1 = I_2 + I_B$$

As  $I_B$  is very small  $I_2 \gg I_B$ , hence  $I_2 \approx I_1$

$$V_{CC} = I_1 R_1 + I_2 R_2$$

$$I_2 = \frac{V_{CC}}{R_1 + R_2}$$

Voltage across  $R_2$  is  $V_B = I_2 R_2$ ,  
 $V_B = \frac{V_{CC} R_2}{R_1 + R_2}$

$$V_B = V_{BE} + V_E$$

$$V_E = V_B - V_{BE}$$

$V_B$  is constant

# Voltage divider bias circuit (approximate analysis)

 


Fig. Voltage divider bias circuit

But  $V_E = I_E R_E$

$$I_E = \frac{V_B - V_{BE}}{R_E} = \frac{V_E}{R_E}$$

$I_E = I_B + I_C \approx I_C$ , since base current is small  
Apply KVL to collector emitter circuit,

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

Since  $I_E \approx I_C$ ,

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

## Problem 4

A voltage divider bias circuit has  $V_{CC}=18V$ ,  $R_1=33k\Omega$ ,  $R_2=12k\Omega$ ,  $R_E=1k\Omega$ ,  $R_C=1.2k\Omega$ ,  $h_{FE}=50$ . Taking  $V_{BE}=0.7V$ , find  $V_E$ ,  $V_{CE}$ ,  $I_C$  and  $V_C$ . Draw the DC load line and locate Q point


 


Fig. Voltage divider bias circuit


# Transistor as a switch: NOT Gate

 

1. A NOT gate simply inverts its input. If the input is HIGH, the output is LOW, and if the input is LOW, the output is HIGH.
2. The input is connected through resistor R2 to the transistor's base.
3. When no voltage is present on the input, the transistor turns off. When the transistor is off, no current flows through the collector-emitter path.
4. Thus, current from the supply voltage ( $V_{cc}$  in the schematic) flows through resistor R1 to the output. In this way, the circuit's output is HIGH when its input is LOW.



# DTL NAND Gate

 

1. When both input A and B are given with 0 V, both of the diodes are in forward biased condition that is in ON condition.
2. Supply voltage will get path to the ground through diode  $D_1$  and  $D_2$ .
3. When both of the inputs are given with +5 V that is logical 1, both of the diodes are in OFF condition and hence supply voltage will appear at the base terminal of the transistor T which makes it switched ON and supply voltage gets a path to the ground through this transistors.

# References

1. [https://www.tutorialspoint.com/amplifiers/methods\\_of\\_transistor\\_biasing.htm](https://www.tutorialspoint.com/amplifiers/methods_of_transistor_biasing.htm)
2. <https://www.britannica.com/technology/transistor>

**Thank You**